 



Digital Electronics

Components

2-to-1 Selector (Multiplexer)




Demultiplexer

 


A **decoder** is a demux with g set to 1.


Level-triggered D Flip-flop

 

Edge-triggered D Flip-flop

 

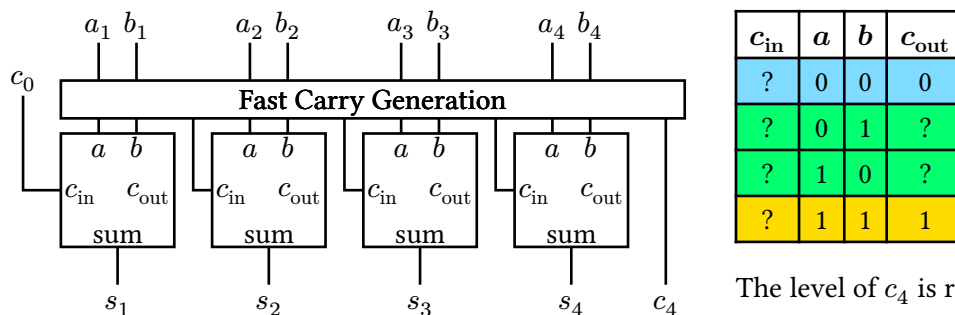In addition, there are the **programmable logic array** and **ROM**. Multiple memory devices can be connected to the same bus with **tristate buffers** which disconnects from the bus when not selected.



The level of c_4 is reduced $8 \rightarrow 5$

Combinatory Logic

Combinatory output depends only on current input.

- **Disjunctive normal form** (sum of product) is the sum minterms.
- **Conjunctive normal form** (product of sum) is the product of maxterms.

Hazards are brief changes in output, multilevel logic can introduce hazards.

- **Static hazards:** output momentarily transitions when isn't supposed to change.
- **Dynamic hazard:** output changes more than once when it's supposed to change once.

Name	Identity
Distribution	$a \cdot (b + c + \dots) = a \cdot b + a \cdot c + \dots$ $a + (b \cdot c \cdot \dots) = (a + b) \cdot (a + c) \cdot \dots$
Absorption	$a + a \cdot b = a$ $a \cdot (a + b) = a$
Consensus	$a \cdot b + \bar{a} \cdot c + b \cdot c = a \cdot b + \bar{a} \cdot c$ $(a + b) \cdot (\bar{a} + c) \cdot (b + c) = (a + b) \cdot (\bar{a} + c)$
DeMorgan's	$\overline{a + b + c + \dots} = \bar{a} \cdot \bar{b} \cdot \bar{c} \cdot \dots$ $\overline{a \cdot b \cdot c \cdot \dots} = \bar{a} + \bar{b} + \bar{c} + \dots$

Logic minification with **K-maps** and the **QM-method**.


1. List all minterms and don't care terms.
2. Merge terms: tick them and write on the next column.
3. Select the minimum covering set of prime implicants.

Sequential Logic

Sequential logic depends on current input and previous state.

- The **ripple counter** is not synchrons, propagation delay build up, limiting maximum clock speed before miscounting happens. We used synchrons counters in lab.
- Counters are used for counting, producing a delay, generating sequences, dividing frequencies.

Shift Registers

 

- It is a synchrons machine because all FFs are connected to the same Clk .
- Q_n is delayed by n clock cycles.


Used as a **serial data link**:

1. Parallel data in
2. Pass through a wire as serial data
3. Parallel data out

Timing Constraints for Asynchronous Input

T_c clock period is the time between rising edges.

 - t_{pc} time after Clk when Q_0 changes
- t_{pd} time after Q_0 when D_1 changes
- t_{su} setup time for the right FF, D_1 needs to settle t_{su} before the next rising edge
- t_{skew} is the range of time Clk reaching all FFs



Requires $T_c \geq \max(t_{pc} + t_{pd} + t_{su} + t_{skew})$

- t_{hold} minimum hold time for the right FF, D_1 cannot update for t_{hold} after Clk

Requires $\min(t_{pc} + t_{pd} + t_{skew}) \geq t_{hold}$

If violated, Q will remain in a **metastable state** until it resolves to a valid state.

$$P(t_{res} > t) = \frac{T_0}{T_c} \exp\left(-\frac{t}{\tau}\right) \quad \text{where } T_0 \text{ and } \tau \text{ are characteristic of the FF.}$$

- $P_{fail} = P(t_{res} > T_c - t_{su})$ is the probability a single FF fails to resolve before the next clock edge.
- $(P_{fail})^n$ is the probability for a **synchroniser** of n cascaded FFs to fail to resolve to a valid state.



If input D_0 changes N times per second, the probability of failure is $t_{su}/T_c \times NP_{fail}$ per second.

$$MTBF = \frac{1}{t_{su}/T_c \times NP_{fail}}$$

Finite State Machines

Moore machine's output only depends state.

  Mealy machine's also directly depend on input.



State assignment is chosen based on what we are trying to optimise: speed or complexity (FFs used).

Sequential State Assignment

abc	$a'b'c'$
000	001
001	010
010	011
011	100
100	101
101	110
110	111
111	100

Sliding State Assignment

abc	$a'b'c'$
000	001
001	011
011	110
110	100
100	000

Shift Register Assignment

$abcde$	$a'b'c'd'e'$
00011	00110
00110	01100
01100	11000
10001	00011

One-hot State Encoding

$abcde$	$a'b'c'd'e'$
00001	00010
00010	00100
00100	01000
00001	00001

State p and q are equivalent if they produce the same bit sequence for the same input sequence.

$$p \equiv q \iff \lambda(p, x) \equiv \lambda(q, x) \wedge \delta(p, x) \equiv \delta(q, x)$$

- λ is the output function
- δ is the next state function

Current state	$x=0$	$x=1$	Output
A	D	C	0
B	F	H	0
C	E	D	1
D	A	E	0
E	C	A	1
F	F	B	1
G	B	H	0
H	C	G	1

We can eliminate identical states with **row matching**.

1. Draw the implication table.
2. (Left) Cross out states that are not equivalent.
3. (Right) The cells not crossed out represents equivalent states.

In example below, $A \equiv D$ and $C \equiv E$


B	D-F C-H						
C							
D	A-D C-E	A-F E-H					
E			C-E A-D				
F			E-F B-D	C-F A-B			
G	B-D C-H	B-F H-H	A-B E-H				
H			C-E D-G	C-C A-G	C-F B-G		
	A	B	C	D	E	F	G

B	D-F C-H						
C							
D	A-D C-E	A-F E-H					
E			C-E A-D				
F			E-F B-D	C-F A-B			
G	B-D C-H	B-F H-H	A-B E-H				
H			C-E D-G	C-C A-G	C-F B-G		
	A	B	C	D	E	F	G

Electricity

Name	Statement
Ohm's law	$V = IR$
Kirchoff's current law	Sum of current entering a junction is zero
Kirchoff's voltage law	In any closed loop the sum of all voltages is zero.

 - **N-type silicon** has extra electrons.
- **p-type silicon** has holes.




A **P-N junction** is a diode.

- When connected with forward bias, the depleted region shrinks so current flows.
- Reverse bias then depleted region grows.

$$\text{logic 0 noise margin} = \max(V_{\text{input low}}) - \max(V_{\text{output low}})$$


$$\text{logic 1 noise margin} = \min(V_{\text{output high}}) - \min(V_{\text{input high}})$$

N-Channel MOSFET

 

Location	Voltage
Body	0V
Source	0V
Drain	$+V_D$
Gate (off)	0V
Gate (on)	$+V_G$

P-Channel MOSFET

 


Location	Voltage
Body	$+V_D$
Source	$+V_D$
Drain	0V
Gate (off)	$+V_G$
Gate (on)	0V

Resistance of the transistor changes non-linearly as gate voltage changes.

N-MOS Inverter


- Slow transition
- High power consumption

 You can find the V_{in} to V_{out} graph using graphical methods.




CMOS Inverter

 - Much sharper transition
- Current flows briefly only when the input changes.



CMOS NOR Gate

 

CMOS NAND Gate

