 



# Digital Electronics

## Components

### 2-to-1 Selector (Multiplexer)




### Demultiplexer

 


A **decoder** is a demux with  $g$  set to 1.


### Level-triggered D Flip-flop

 

### Edge-triggered D Flip-flop

 

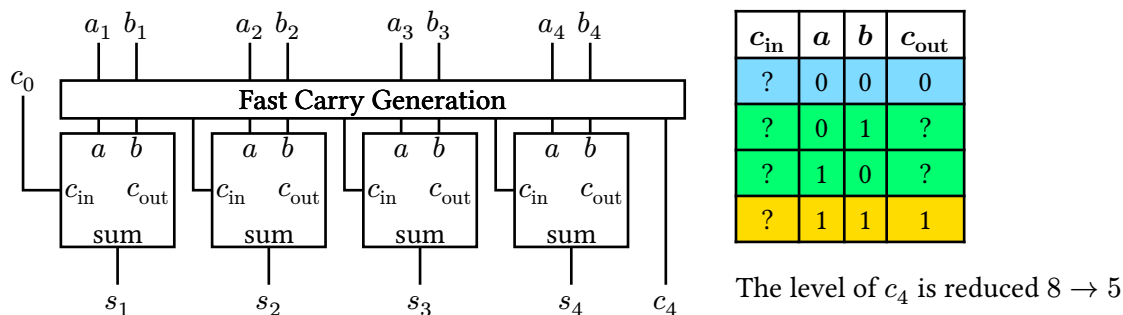In addition, there are the **programmable logic array** and **ROM**. Multiple memory devices can be connected to the same bus with **tristate buffers** which disconnects from the bus when not selected.



## Combinatory Logic

**Combinatory output** depends only on current input.

- **Disjunctive normal form** (sum of product) is the sum minterms.
- **Conjunctive normal form** (product of sum) is the product of maxterms.

**Hazards** are brief changes in output, multilevel logic can introduce hazards.

- **Static hazards:** output momentarily transitions when isn't supposed to change.
- **Dynamic hazard:** output changes more than once when it's supposed to change once.

Name	Identity
Distribution	$a \cdot (b + c + \dots) = a \cdot b + a \cdot c + \dots$ $a + (b \cdot c \cdot \dots) = (a + b) \cdot (a + c) \cdot \dots$
Absorption	$a + a \cdot b = a$ $a \cdot (a + b) = a$
Consensus	$a \cdot b + \bar{a} \cdot c + b \cdot c = a \cdot b + \bar{a} \cdot c$ $(a + b) \cdot (\bar{a} + c) \cdot (b + c) = (a + b) \cdot (\bar{a} + c)$
DeMorgan's	$\overline{a + b + c + \dots} = \bar{a} \cdot \bar{b} \cdot \bar{c} \cdot \dots$ $\overline{a \cdot b \cdot c \cdot \dots} = \bar{a} + \bar{b} + \bar{c} + \dots$

Logic minification with **K-maps** and the **QM-method**.


1. List all minterms and don't care terms.
2. Merge terms: tick them and write on the next column.
3. Select the minimum covering set of prime implicants.

## Sequential Logic

**Sequential logic** depends on current input and previous state.

- The **ripple counter** is not synchronous, propagation delay build up, limiting maximum clock speed before miscounting happens. We used synchronous counters in lab.
- Counters are used for counting, producing a delay, generating sequences, dividing frequencies.

### Shift Registers

 

- It is a synchronous machine because all FFs are connected to the same  $Clk$ .
- $Q_n$  is delayed by  $n$  clock cycles.

Used as a **serial data link**:

1. Parallel data in
2. Pass through a wire as serial data
3. Parallel data out

## System Timing